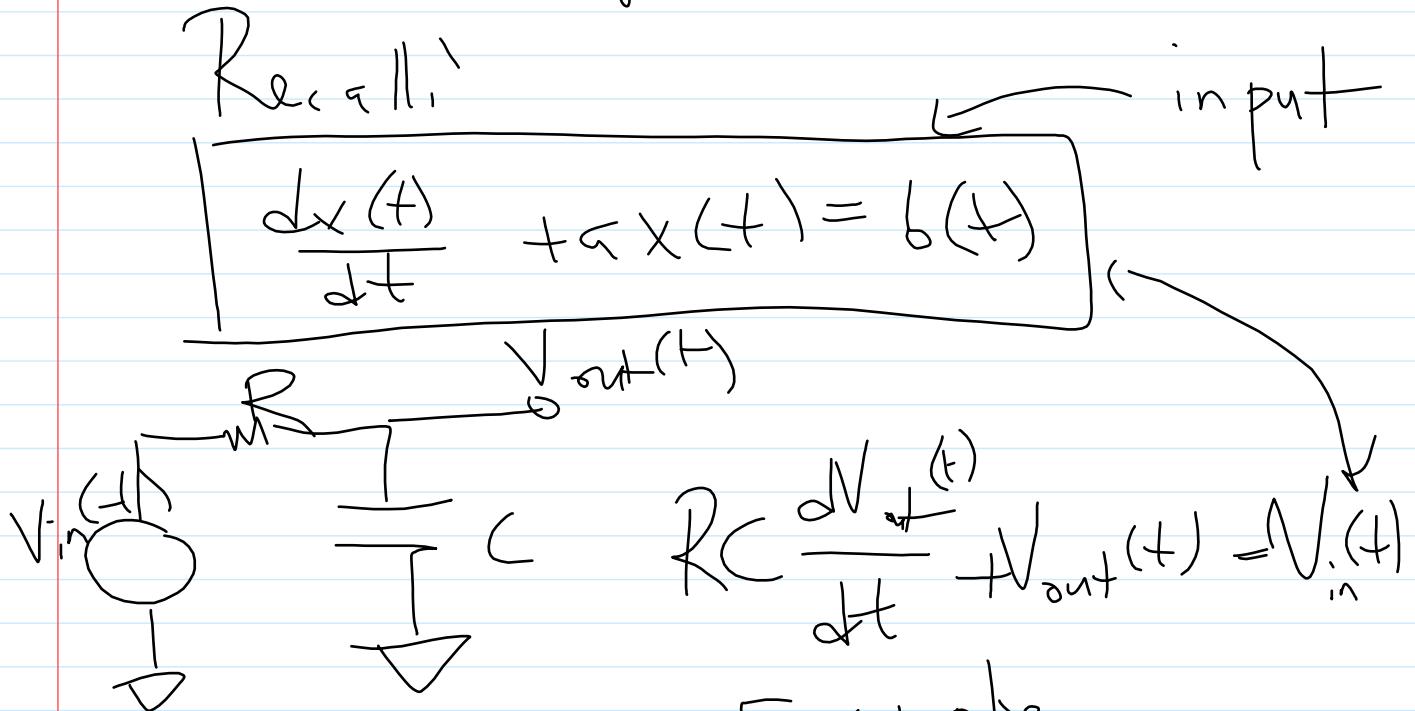


Phasors

I. The Big Picture (high Level)

Why have we been learning about diff eq, but jump to complex H's and "phasors"

⇒ Want to make solving diff eq easier



Example

$$x(t) = e^{-\alpha(t-t_0)} x_0 + \int_{t_0}^t e^{-\alpha(t-t')} u(t') dt'$$

$$X(t) = X_0 e^{\{t\} \omega_p(t)}$$


X_0 + $\{t\} \omega_p(t)$
 $(t'$ is a dummy variable)

Connection to complex H's:

Plug in $e^{\{t\} \omega_p(t)}$ (for some reason)

w/ appropriate boundary conditions
 (e.g. $t \rightarrow \infty$ so e^{-at})
 vanishes

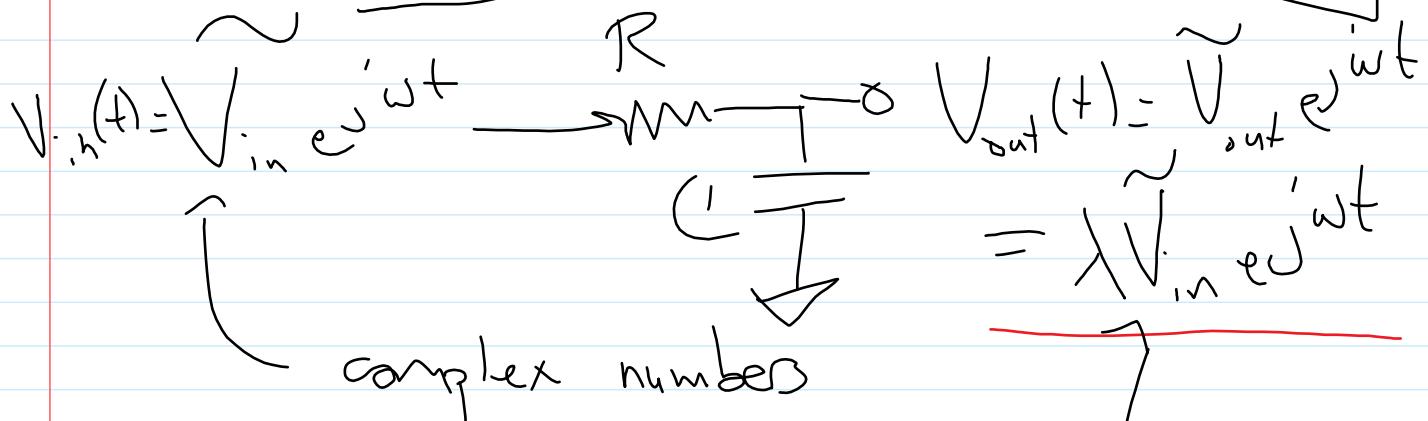\Rightarrow We get a steady state response that is just a scaled version of input,



Exploiting eigenfn property of

Exponentials under differentiation

Suggest we can skip the integral

$$RC \frac{dV_{out}}{dt} + V_{out} = V_{in}$$

$$\tilde{V}_{out}(+) = \tilde{V}_{out} e^{j\omega t}$$

$$\tilde{V}_{in}(+) = \tilde{V}_{in} e^{j\omega t}$$

$$RC(j\omega \tilde{V}_{out}) + \tilde{V}_{out} = \tilde{V}_{in} e^{j\omega t}$$

$$\tilde{V}_{out} (1 + j\omega RC) = \tilde{V}_{in}$$

$$\tilde{V}_{out} = \tilde{\lambda} \tilde{V}_{in} = \frac{1}{1 + j\omega RC} \tilde{V}_{in}$$

Some Notes

* The gross integral $\int e^{-\alpha(t-t')} u(t') dt'$


works for any input, not just $e^{j\omega t}$

* But integrals are hard

↳ What if we wanted to look
at a more complicated diff eq
(e.g. more complex circuit)

→ take hint of eigen
property of $e^{j\omega t}$

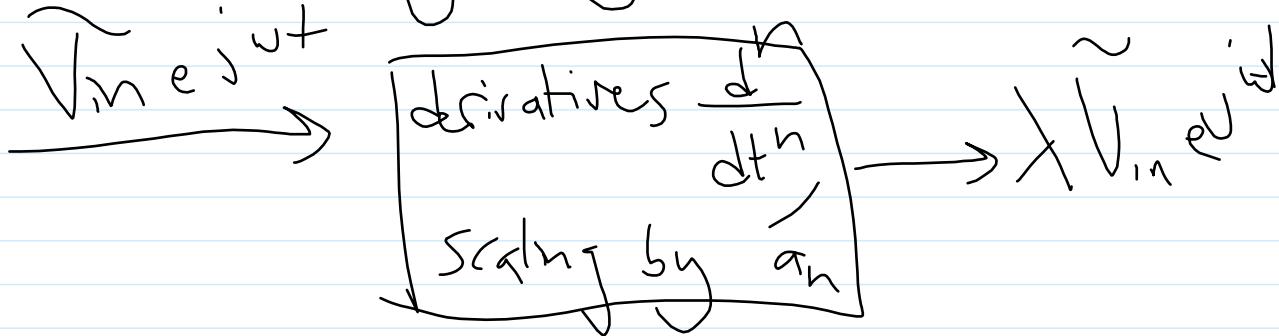Expect method of plug in
 $\tilde{V}_{in} e^{j\omega t}$, get out $\tilde{V}_{out} e^{j\omega t}$
to work for any diff eq only
containing derivatives and
multiplying by constants



But why $e^{j\omega t}$???

The (short) answer:

we care about sinusoidal inputs

(e.g. 60 Hz AC from wall)

$$V_n \cos(\omega t + \varphi) = \operatorname{Re} \{ V_n e^{j\omega t} \}$$

\tilde{V}_{in} is called the **phasor** of

the signal $V_n(t)$

$$\tilde{V}_{in} = V_{in} e^{j\varphi} \quad \begin{matrix} \leftarrow \text{phase of} \\ \text{the signal} \end{matrix}$$

\leftarrow amplitude of signal

$$V_n \cos(\omega t + \varphi) = V_{in} e^{j(\omega t + \varphi)} + V_{in} e^{-j(\omega t + \varphi)}$$

$$= (V_{in} e^{j\varphi}) e^{j\omega t} + (V_{in} e^{-j\varphi}) e^{-j\omega t}$$

$$= \frac{(V_{in} e^{j\omega t})e^{-j\omega t} + (V_{in} e^{-j\omega t})e^{j\omega t}}{2}$$

$$= \frac{\tilde{V}_{in} e^{j\omega t} + \tilde{V}_{in} e^{-j\omega t}}{2}$$

Clearly, plugging in $\tilde{V}_{in} e^{j\omega t}$ is easier than $V_{in} \cos(\omega t + \phi)$

Ex:

$$RC \frac{d\tilde{V}_{out}(t)}{dt} + V_{out}(t) = V_{in} \cos(\omega t + \phi)$$

same equation

$$\begin{aligned} & RC \frac{d}{dt} \operatorname{Re}\{\tilde{V}_{out} e^{j\omega t}\} + \operatorname{Re}\{\tilde{V}_{out} e^{j\omega t}\} \\ &= \operatorname{Re}\{\tilde{V}_{in} e^{j\omega t}\} \quad (1) \end{aligned}$$

It can be shown (using linearity mainly) that solving the

equation for complex exp.

$$(2) \underbrace{RC \frac{d}{dt} (\tilde{V}_{out} e^{j\omega t}) + V_{out} e^{j\omega t}}_{= V_{in} e^{j\omega t}}$$

also solves the eqn w/ cosine

(Solving simpler eqn 2 \rightarrow solves 1)

II. The Mechanics

(what you [↑] need to know
definitely)

Motivation for phasor analysis procedure

* even setting up the diff eq can be
hard

* would like an even simpler
procedure where we skip the
diff eq ← what???

Look at R, L, C :

$$C = \frac{1}{T}$$

$$I_c(t) = C \frac{dV_c(t)}{dt}$$

Put in $\tilde{V}_c e^{j\omega t}$, solve
for $\tilde{I}_c e^{j\omega t}$



Same as if we had put in

$$V_c(t) = R_o \{ \tilde{V}_c e^{j\omega t} \} = V_c \cos(\omega t + \phi)$$

~~$$\tilde{I}_c e^{j\omega t} = C \frac{d}{dt} (\tilde{V}_c e^{j\omega t})$$~~

~~$$= C j \omega \tilde{V}_c e^{j\omega t}$$~~

$$\boxed{\tilde{V}_c = \frac{1}{j\omega C} \tilde{I}_c = Z_C \tilde{I}_c}$$

Similarly, inductors:

$$V_{in} = \tilde{V}_{in} e^{j\omega t}$$

$$V_L = L \frac{dI_L}{dt}$$

$$\begin{aligned} \tilde{V}_{\text{out}} e^{j\omega t} &= L \frac{d}{dt} \tilde{I}_L e^{j\omega t} \\ \boxed{\tilde{V}_L} &= j\omega L \tilde{I}_L = Z_L \tilde{I}_L \end{aligned}$$

Each d.c.t. element contributes its own diff eq of sorts to the final diff eq (for sinusoidal inputs)

→ Then setting up the full diff eq (e.g., RC d.c.t from earlier)



Amounts to working with:


* "phasor $\tilde{I}-V$ " $\Rightarrow \tilde{V} = Z \tilde{I}$

* "complex valued resistors"

⇒ impedances

$$Z_R = R$$

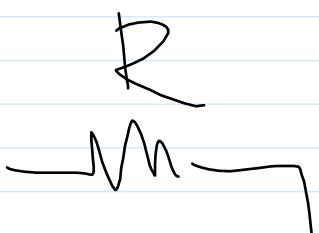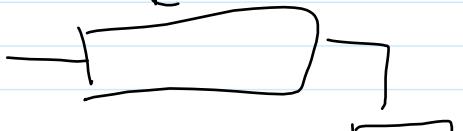

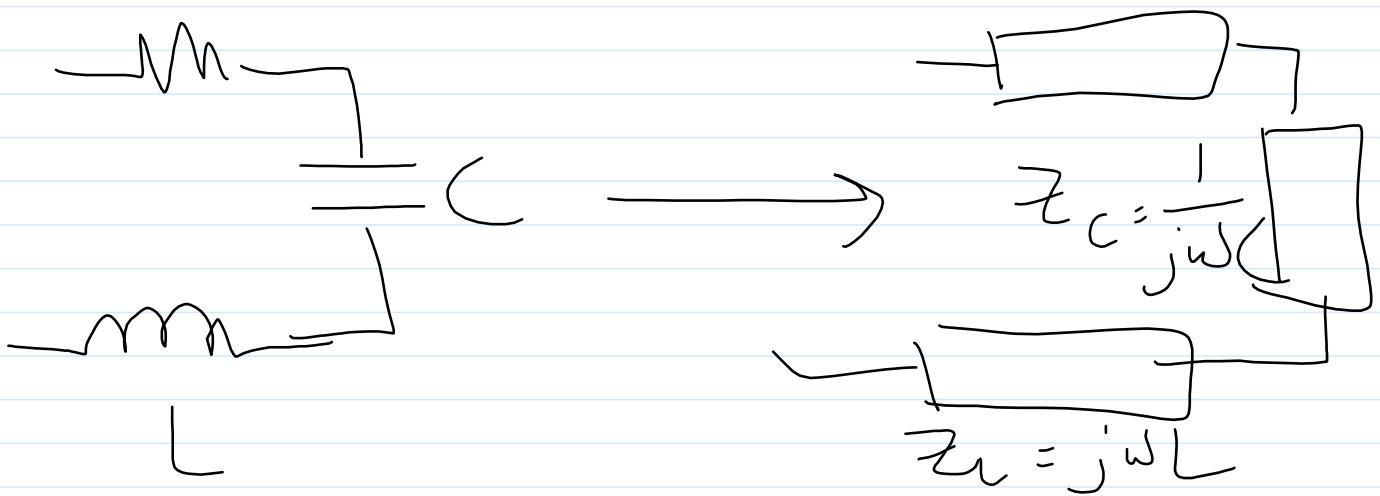

From here; use ckt solving techniques
from 16A!

~~5~~ 5-step method for ~~phasor~~
phasor analysis

① Cosine reference; Convert all
signals into cosines

$$V_o \cos(\omega t + \phi) = \text{Re} \left\{ V_o e^{j\phi} e^{j\omega t} \right\}$$

\sim

V_o phasor

② Transform ckt to phasor
domain;

$$V(t) \longrightarrow \tilde{V} = V_0 e^{j\phi_v}$$

$$I(t) \longrightarrow \tilde{I} = I_0 e^{j\phi_i}$$

$$R, L, C \longrightarrow Z_R = R$$

$$\frac{1}{j} = -j$$

$$Z_L = j\omega L$$

$$\frac{1}{j} \times \frac{j}{j} = \frac{j}{j^2} = -j \quad = \frac{-j}{\omega C}$$

③ Use KCL, KVL in phasor domain.

④ Solve for unknowns.

⑤ Transform back to time domain

$$V_0 e^{j\phi} \rightarrow V_0 \cos(\omega t + \phi)$$

Dis 2B Worksheet

Tuesday, June 30, 2020 12:02 PM


2 Phasor Analysis

Any sinusoidal time-varying function $x(t)$, representing a voltage or a current, can be expressed in the form

$$x(t) = \Re[X e^{j\omega t}], \quad (1)$$

where X is a time-independent function called the phasor counterpart of $x(t)$. Thus, $x(t)$ is defined in the time domain, while its counterpart X is defined in the phasor domain.

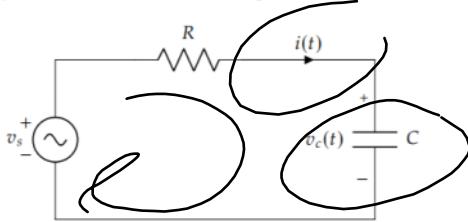The phasor analysis method consists of five steps. Consider the RC circuit below.



The voltage source is given by

$$v_s(t) = 12 \sin\left(\omega t - \frac{\pi}{4}\right), \quad (2)$$


with $\omega = 1 \times 10^3 \frac{\text{rad}}{\text{s}}$, $R = \sqrt{3} \text{k}\Omega$, and $C = 1 \mu\text{F}$.

Our goal is to obtain a solution for $i(t)$ with the sinusoidal voltage source $v_s(t)$.

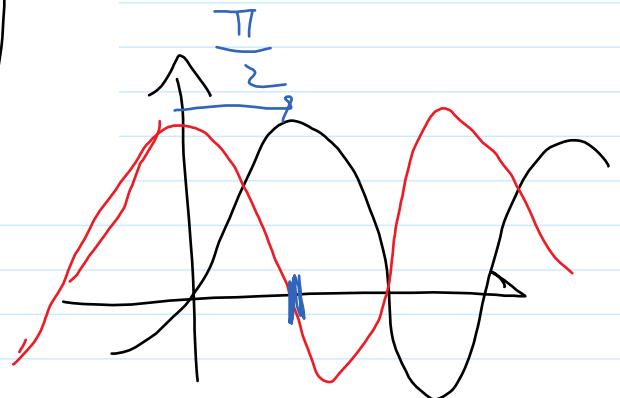a) Step 1: Adopt cosine references

All voltages and currents with known sinusoidal functions should be expressed in the standard cosine format. Convert $v_s(t)$ into a cosine and write down its phasor representation \bar{V}_s .

$$v_s(t) = 12 \sin\left(\omega t - \frac{\pi}{4}\right)$$



convert cos → sine

Subtract $\frac{\pi}{2}$ ← Shift by $\frac{\pi}{2}$ "forward"

$$v_s(t) = 12 \cos\left(\omega t - \frac{\pi}{4} - \frac{\pi}{2}\right)$$

$$= 12 \cos\left(\omega t - \frac{3\pi}{4}\right)$$

$$= \Re \left\{ V_s e^{j\phi_s} e^{j\omega t} \right\}$$

$$\boxed{V_s e^{j\phi_s} e^{j\omega t}}$$


$$\Rightarrow \boxed{\tilde{V}_S = |Z_c| e^{-j\frac{3\pi}{4}}}$$

b) Step 2: Transform circuits to phasor domain

The voltage source is represented by its phasor \tilde{V}_S . The current $i(t)$ is related to its phasor counterpart \tilde{I} by

$$i(t) = \Re[\tilde{I}e^{j\omega t}]$$

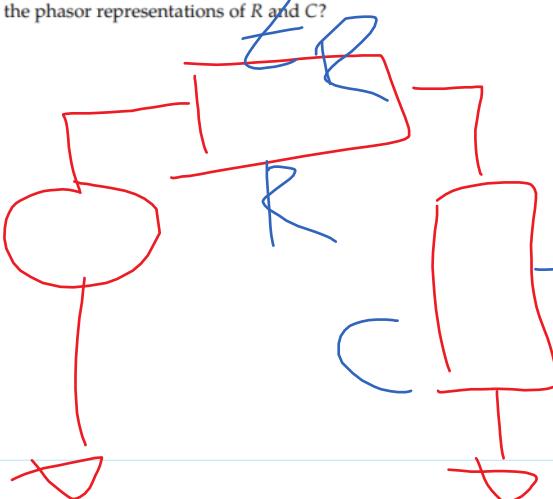What are the phasor representations of R and C ?




$$\begin{aligned} V_s(t) &\rightarrow \tilde{V}_S \\ i(t) &\rightarrow \tilde{I} \end{aligned}$$

$$Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$

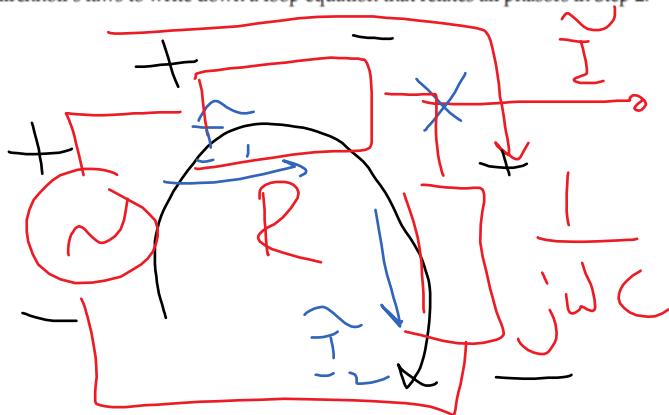c) Step 3: Cast KCL and/or KVL equations in phasor domain

Use Kirchhoff's laws to write down a loop equation that relates all phasors in Step 2.



$$\begin{aligned} \text{KCL: } & \frac{\tilde{V}_S}{I} = \frac{\tilde{V}_R}{I} = \frac{\tilde{V}_C}{I} \\ -\tilde{V}_S + \tilde{V}_R + \tilde{V}_C &= 0 \\ \tilde{V}_S &= I \left(Z_R + Z_C \right) \end{aligned}$$

$$\begin{aligned} \tilde{V}_S &= 12 e^{j \frac{3\pi}{4}} = \frac{\tilde{V}_S}{I} \left(R + \frac{1}{j\omega C} \right) \\ \Rightarrow \frac{\tilde{V}_S}{I} &= \frac{\tilde{V}_S}{R + \frac{1}{j\omega C} + j\omega C} \end{aligned}$$

$$\boxed{\frac{\tilde{V}_S}{I} = \frac{j\omega C \tilde{V}_S}{1 + j\omega RC}}$$

$$\begin{aligned} \tilde{V}_C &= Z_C \frac{\tilde{V}_S}{I} = \frac{1}{j\omega C} \times j\omega C \tilde{V}_S \\ \Rightarrow \frac{\tilde{V}_C}{I} &= \frac{\tilde{V}_S}{1 + j\omega RC} \end{aligned}$$

Try
r.h.s. Hand

$$\Rightarrow \left(\tilde{V}_c = \frac{\tilde{V}_s}{1+j\omega RC} \right)$$

Voltage divider

d) Step 4: Solve for unknown variables


Solve the equation you derived in Step 3 for \tilde{I} and \tilde{V}_c . What are the polar forms of \tilde{I} ($Ae^{j\theta}$, where A is a positive real number) and \tilde{V}_c ?

$$\tilde{I} = \frac{\tilde{V}_s j\omega C}{1+j\omega RC} = \frac{j12e^{-j\frac{3\pi}{4}} \left(10^3 \frac{rad}{s} \right) \times (1\mu F)}{1+j\left(10^3 \right) \left(1\mu F \right) \left(\sqrt{3} k\Omega \right)}$$

$$= \frac{12j e^{-j\frac{3\pi}{4}}}{1 + j\sqrt{3}}$$

$$(polar) = \frac{12j e^{-j\frac{3\pi}{4}}}{\sqrt{1^2 + \sqrt{3}^2}} e^{j \arctan(\sqrt{3}, 1)}$$
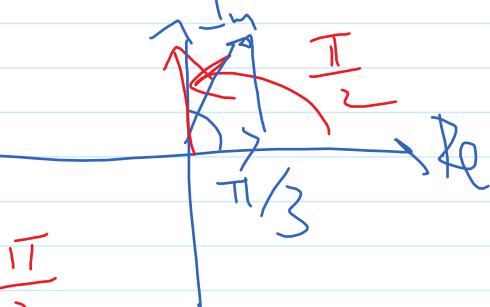
$$= \frac{12j e^{-j\frac{3\pi}{4}}}{2e^{j\pi/3}} mA$$



$$= \frac{12e^{-j\frac{3\pi}{4}} e^{j\frac{\pi}{2}}}{2e^{j\pi/3}}$$

$$= \frac{6e^{-j\frac{\pi}{4}}}{2e^{j\pi/3}} = -\frac{3}{2} e^{-j\frac{\pi}{4}} = -\frac{3}{2} e^{-j\frac{\pi}{3}}$$

$$\approx -17\pi$$

see if it matches! (it should)

$$\tilde{I} = 6e^{-j\frac{7\pi}{12}}$$

$$\tilde{V}_c = \frac{\tilde{I}}{1+j\omega RC} = \frac{12e^{j\frac{3\pi}{4}}}{1+j\sqrt{3}} = \frac{12e^{j\frac{3\pi}{4}}}{2e^{j\pi/3}}$$

$$\tilde{I}_c = 6e^{-j\frac{13\pi}{12}}$$

$$-\frac{3\pi}{4} - \frac{\pi}{3} = \frac{-13\pi}{12}$$

e) Step 5: Transform solutions back to time domain

To return to time domain, we apply the fundamental relation between a sinusoidal function and its phasor counterpart. What is $i(t)$ and $v_c(t)$? What is the phase difference between $i(t)$ and $v_c(t)$?

$$i(t) = \Re \left\{ \tilde{I} e^{j\omega t} \right\}$$

$$= \frac{\tilde{I} e^{j\omega t}}{2} + \frac{\tilde{I} e^{j\omega t}}{2} \text{ mA}$$

$$= \frac{6e^{-j\frac{7\pi}{12}} e^{j\omega t} + 6e^{j\frac{13\pi}{12}} e^{j\omega t}}{2} \text{ mA}$$

$$= \frac{12 \cos(\omega t - \frac{7\pi}{12})}{2} \text{ mA}$$

$$i(t) = 6 \cos(\omega t - \frac{7\pi}{12}) \text{ mA}$$

$$V_o \cos(\omega t + \phi) = \operatorname{Re} \{ V_o e^{j\phi} e^{j\omega t} \}$$

$$\tilde{V}_o = 6 e^{-j \frac{13\pi}{12}}$$

$$\Rightarrow \boxed{V_c(t) = 6 \cos\left(\omega t - \frac{13\pi}{12}\right) \text{ V}}$$